Tabela de Transição de Estados

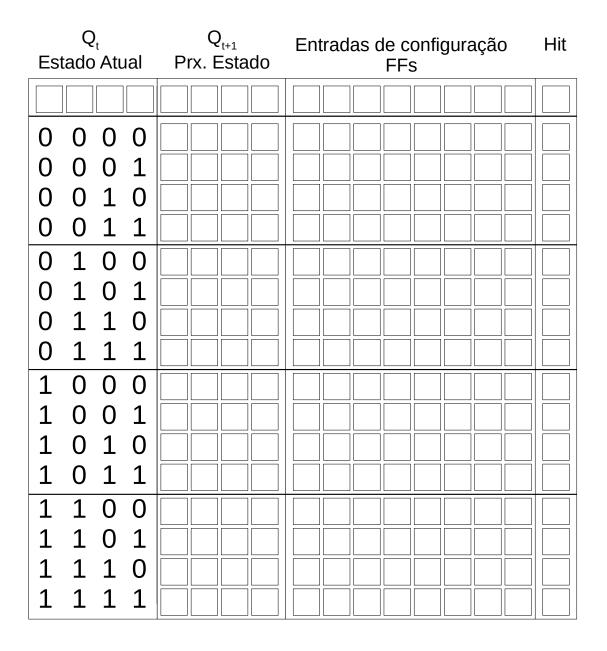


Tabela de Transição dos Flip-flops

Qn	Qn+1	J	K
0	0	0	Χ
0	1	1	Χ
1	0	Χ	1
1	1	Χ	0

Qn	Qn+1	Т
0	0	0
0	1	1
1	0	1
1	1	0

Qn	Qn+1	D
0	0	0
0	1	1
1	0	0
1	1	1

Mapas Karnaugh 4

